



## Midterm# 1

Thur., Oct. 16, 2014, at 9:45AM 10:55am, in class.

Open books and notes – anything on paper. No electronic aids allowed *except* for laptops or tablets to display electronic copies of the text by Roth. You are not allowed to display *anything* else on a laptop or tablet. No phones.

### 1. Conversion Between Different Number Representations [12 pts.]

- (a) Convert the following binary numbers to decimal [1 pts]:
  - i. 101.101
- (b) Convert the following decimal numbers to binary [1 pts]. Truncate after 12 bits beyond the binary point.
  - i. 666.666
- (c) Perform the following number conversions [1 pts]:
  - i. Binary 1010001101110111101101001110 to hexadecimal
  - ii. Hexadecimal 67AC789AB6BF786 to binary.
- (d) Perform the following number conversions[3 pts]:
  - i.  $665_7$  (base 7) to base 5
- (e) Give the negative of the following numbers in two's complement notation (length is 8 bits) [3 pts].
  - i. 11101111
  - ii. 00010000
- (f) Suppose that the following bits represent positive and negative numbers in two's complement notation. Perform the operation indicated, keeping the length at 8 bits. Give the result in binary [3 pts].
  - i.  $11111110_2 + 00111111_2$ .
  - ii.  $00111111_2 \times 11111110_2$ .

**2. Boolean Functions, Truth Tables, Logic Minimization, Two-Level Forms and Binary Decision Diagrams [40 pts.]**

Consider a boolean function  $f(a, b, c, d)$ . Suppose that the function is 1 if


- There is a single 1 among the inputs, or
- There is a single 0 among the inputs, or
- There are exactly two 1's among the inputs


and it is 0 otherwise.


- (a) Write down a truth table for the function [2 pts.]
- (b) Using a Karnaugh map, provide a minimal sum-of-products (AND-OR) expression. [3 pts.]
- (c) Using a Karnaugh map, provide a minimal product-of-sums (OR-AND) expression. [3 pts.]
- (d) Provide a minimal NAND-NAND expression [2 pts.].
- (e) Provide a minimal OR-NAND expression [2 pts.].
- (f) Provide a minimal NOR-OR expression [2 pts.].
- (g) Provide a minimal NOR-NOR expression [2 pts.].
- (h) Provide a minimal AND-NOR expression [2 pts.].
- (i) Provide a minimal NAND-AND expression [2 pts.].
- (j) Provide a AND-XOR expression (with no negations) [10 pts.].
- (k) Draw a reduced Binary Decision diagram for the function [10 pts.].

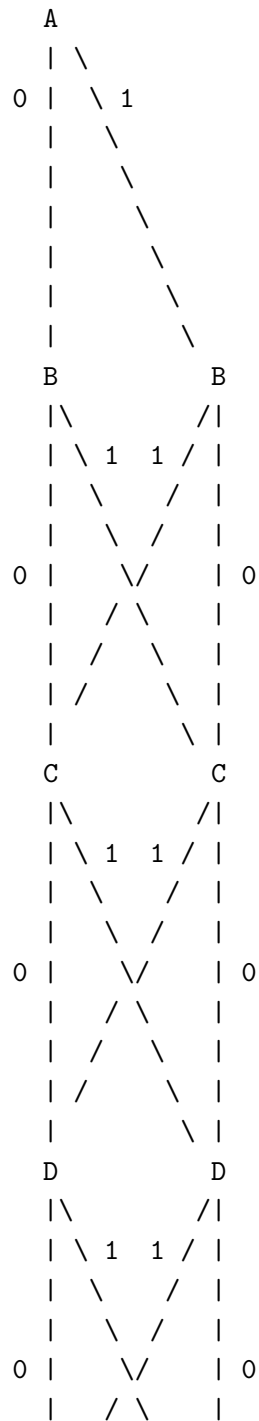3. Expressions from Binary Decision Diagrams [24 pts.]

Provide an expression for the function of this BDD.



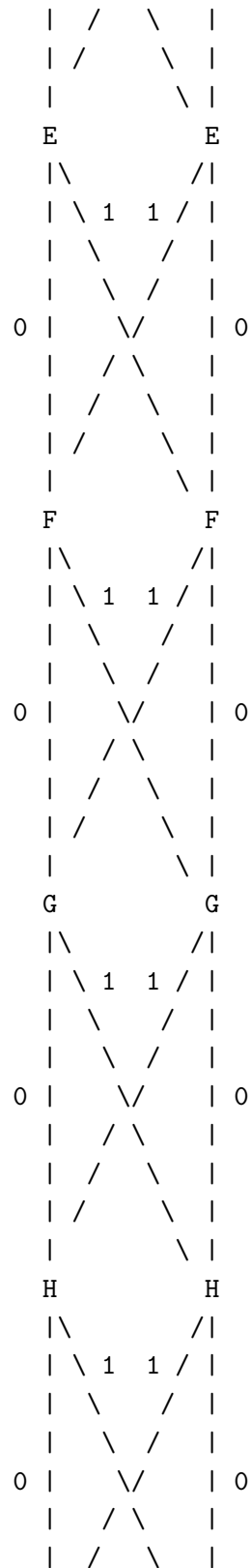

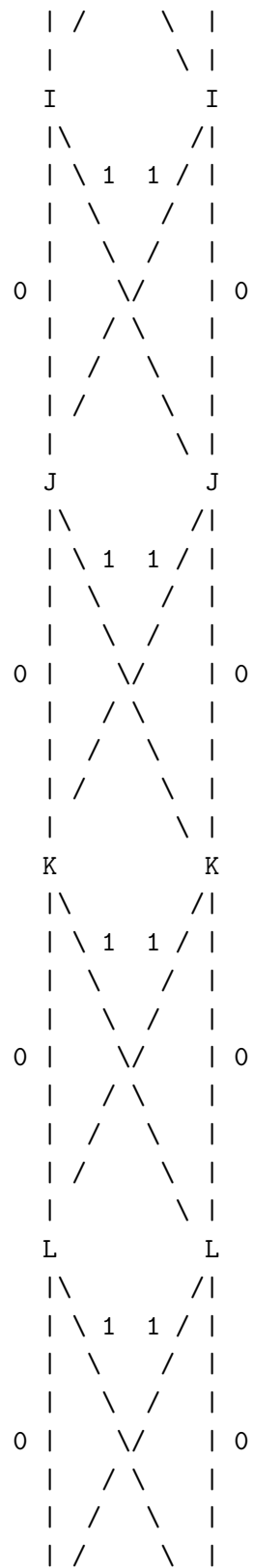

	\
-----	-----
0	1
-----	-----

4. **Timing Analysis** [24 pts.]

Compute the arrival times at  $f_1$ ,  $f_2$ , and  $f_3$  for each input combination for the following circuit. Assume a delay of 1 for each gate. Assume that the bubbles have *no* delay.

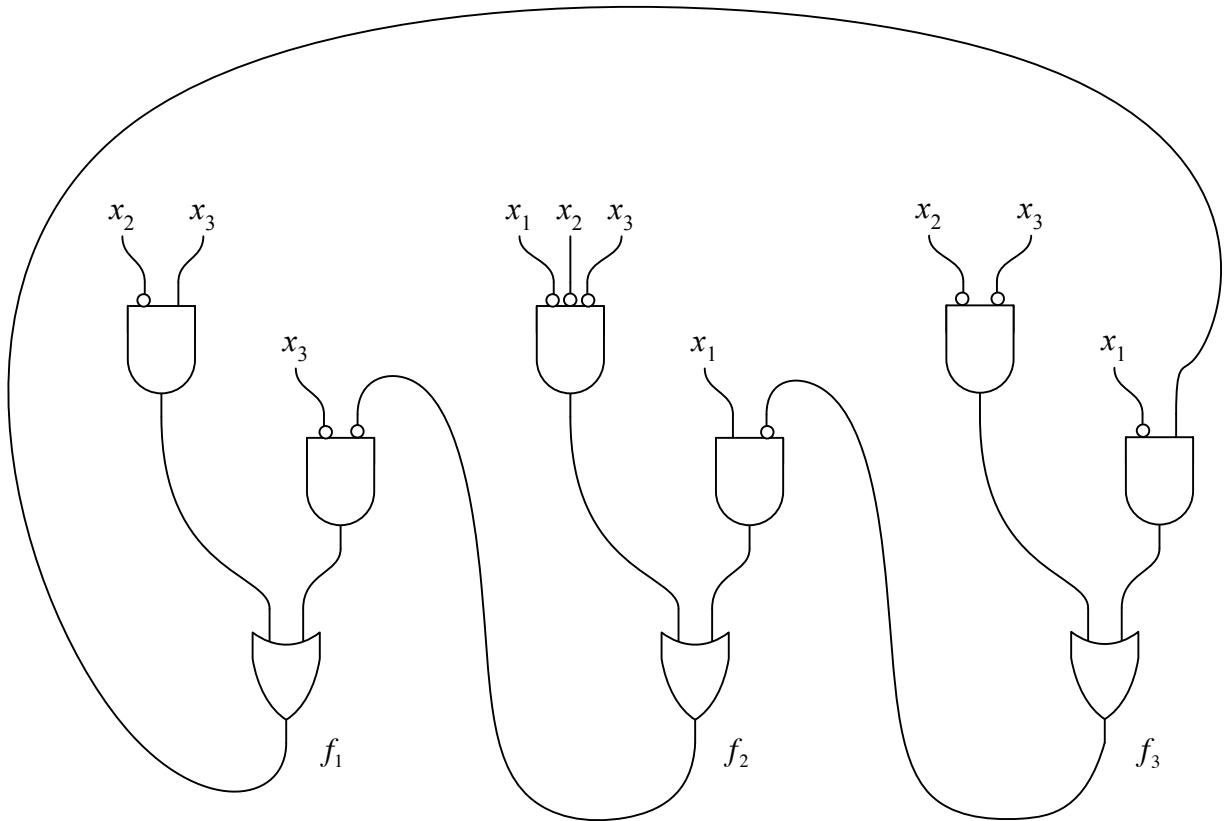


Figure 1: Circuit for Timing Analysis.